
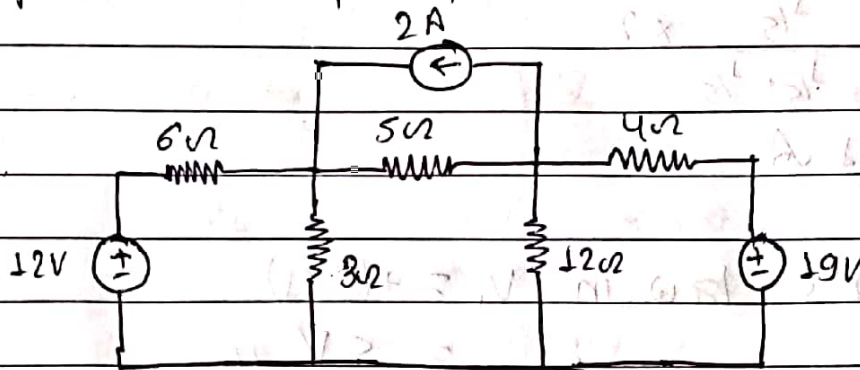


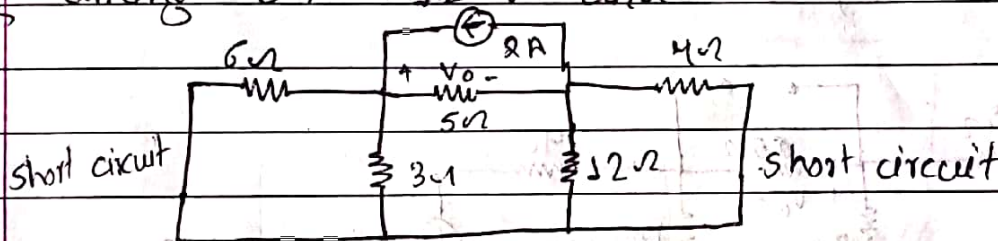6) Determine V_0 in the circuit below using the superposition principle




Case 1 Turning off 12V and 10V




Now, $6\Omega // 3\Omega$ and $12\Omega // 4\Omega$

$$R_{eq} = \frac{6 \times 3}{6 + 3} = 2\Omega$$
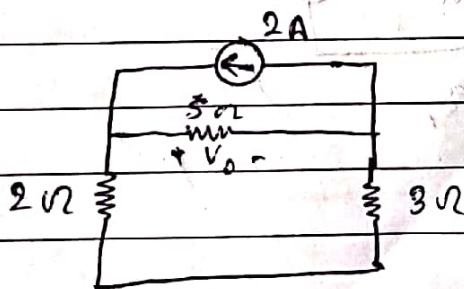
$$R_{eq} = \frac{12 \times 4}{12 + 4} = 3\Omega$$



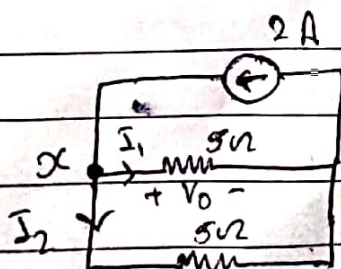2Ω and 3Ω are in series,
 $R_{eq} = 2 + 3 = 5\Omega$



At point x using current divider rule,



$$I_1 = \frac{\frac{1}{5}}{\frac{1}{5} + \frac{1}{5}} \times 2$$

$$= 1 \text{ A}$$


Now,

Using Ohm's law in $V_1 = +(5 \times 1)$
 $= 5 \text{ V}$

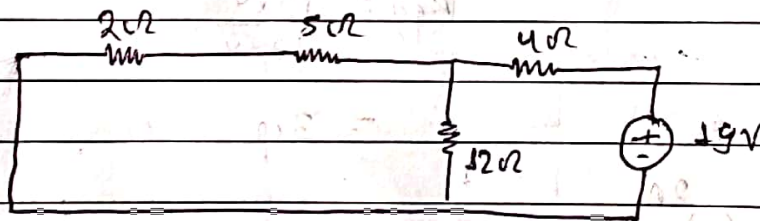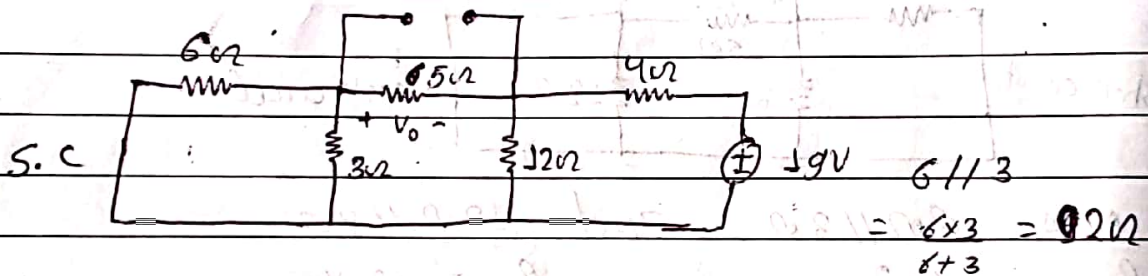Case 2) Consider 19 V , turn off 2 A and 12 V




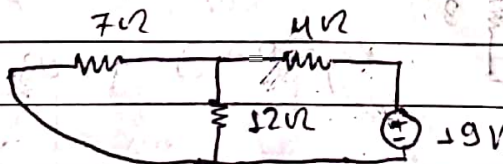2Ω and 5Ω are in series,
 $2+5 = 7\Omega$



7Ω and 12Ω are parallel,
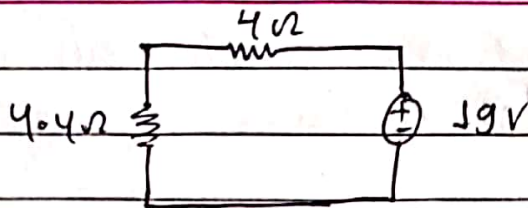
$$R_{eq} = \frac{7 \times 12}{7 + 12} = 4.42 \Omega$$




Using voltage divider rule,

$$V_{4.4\Omega} = \frac{4.4\Omega}{4 + 4.4\Omega} \times 19$$


$$= 9.97 \text{ V}$$

Turning off 2A and 19V

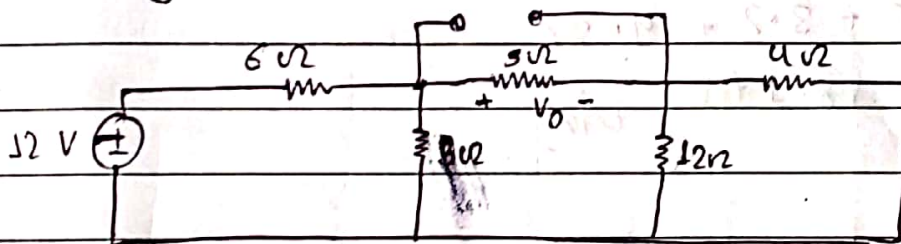


4Ω and 12Ω are in parallel so,

$$R_{eq} = 3\Omega$$

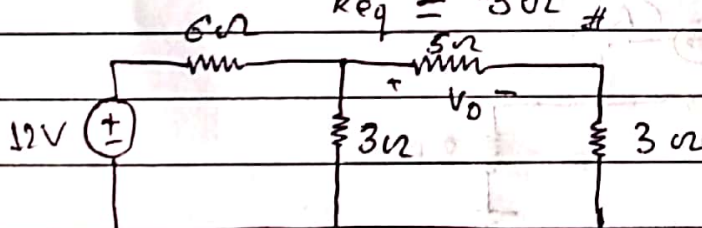


5Ω and 3Ω are in series so,

$$R_{eq} = 5 + 3 = 8\Omega$$

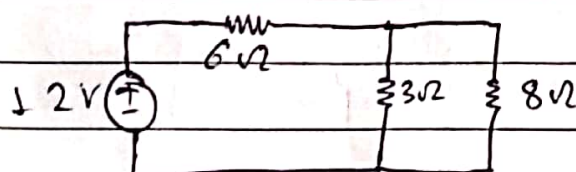

3Ω and 8Ω are in parallel

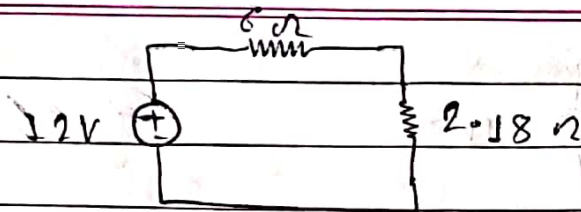

Using vol. D.R. at,

$$V_{2.18} = \frac{2.18}{6 + 2.18} \times 12$$

$$= 3.2 \text{ V}$$


Using S.T

$$V_0 = 0.5 + 3.2 + 9.97$$


$$= 13.77 \text{ V}$$

Ans.

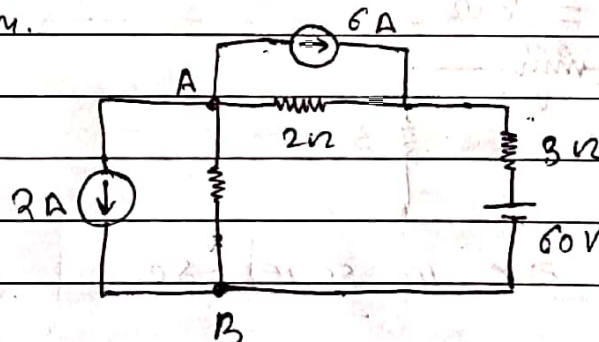2) Find the voltage across 5 ohm using superposition Theorem.



Turn off 2A and 60V

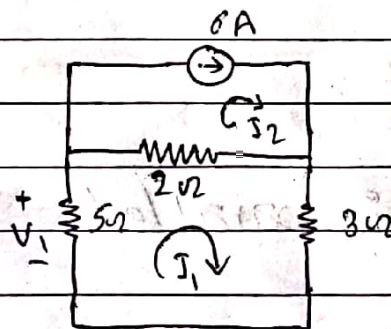

$$I_2 = 6A$$

using KVL in mesh ①

$$-3I_1 - 2(I_1 - I_2) - V_1 = 0$$

$$V_1 + 2(I_1 + 6) + 3I_1 = 0$$

$$I_1 = -1.2A$$


Using ohm's law,

$$V_1 = +I_1 \times 5$$

$$= -1.2 \times 5$$

$$= -6V$$

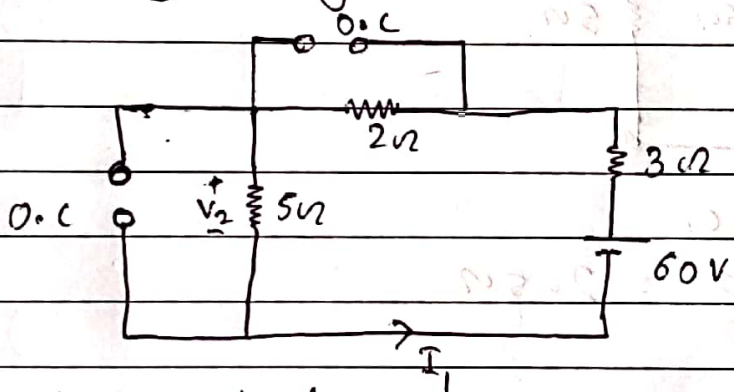considering only 60V and turn off 6A and 2A



Applying KVL,

$$-5I + 60 - 3I - 2I = 0$$

$$-10I = -60$$

$$I = 6A$$


Using ohm's law,

$$V_1 = I \times 5\Omega$$


$$= 6 \times 5$$

$$= 30V$$

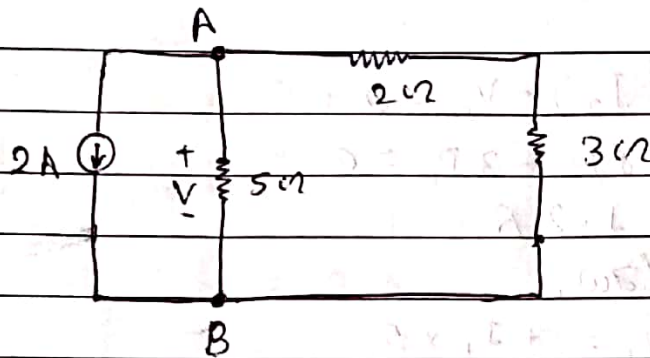Considering only 2A and turning off 6A and 60V




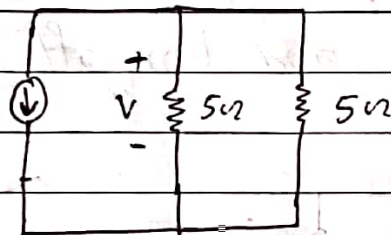2Ω and 3Ω are in series, so,
 $R_{eq} = 2 + 3 = 5\Omega$



5Ω || 5Ω so,
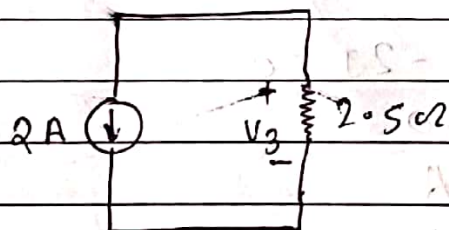
$$R_{eq} = \frac{5 \times 5}{5 + 5} = 2.5\Omega$$



$$\text{Now, } V_3 = -2.5 \times 2 = -5V$$

Now, using superposition Theorem

$$\begin{aligned} V &= V_1 + V_2 + V_3 \\ &= -5 + 30 + -6 \\ &= 19V \end{aligned}$$